BHARAT BHATI

Roll No: 2501730452

Subject: Nand2Tetris

Course: B.Tech CSE AIML

Section: G

Bharat Bhati


1. And.hdl (Project

1) Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/And.hdl
/**  * And
gate:
* if (a and b) out = 1, else out = 0
 */
CHIP And {
    IN a, b;
    OUT out;

PARTS:
    Nand(a=a, b=b, out=nand1);
    Nand(a=nand1, b=nand1 ,out=out);
}
```

Screenshot (Hardware Simulator output):

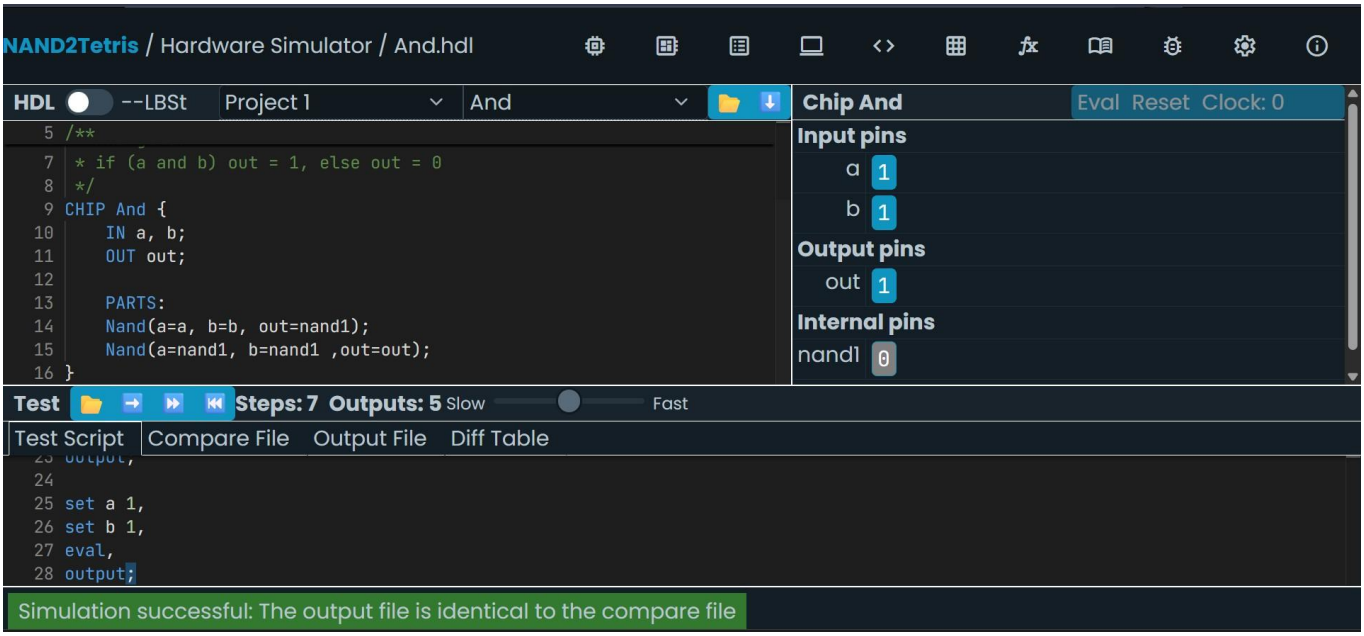

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
```


2. Not.hdl (Project 1)

Code:

```
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Not.hdl
/**  * Not
gate:
* if (in) out = 0, else out = 1
 */
CHIP Not {
    IN in;
    OUT out;

    PARTS:
    Nand(a=in,b=in,out=out);
}
```

Screenshot (Hardware Simulator output):

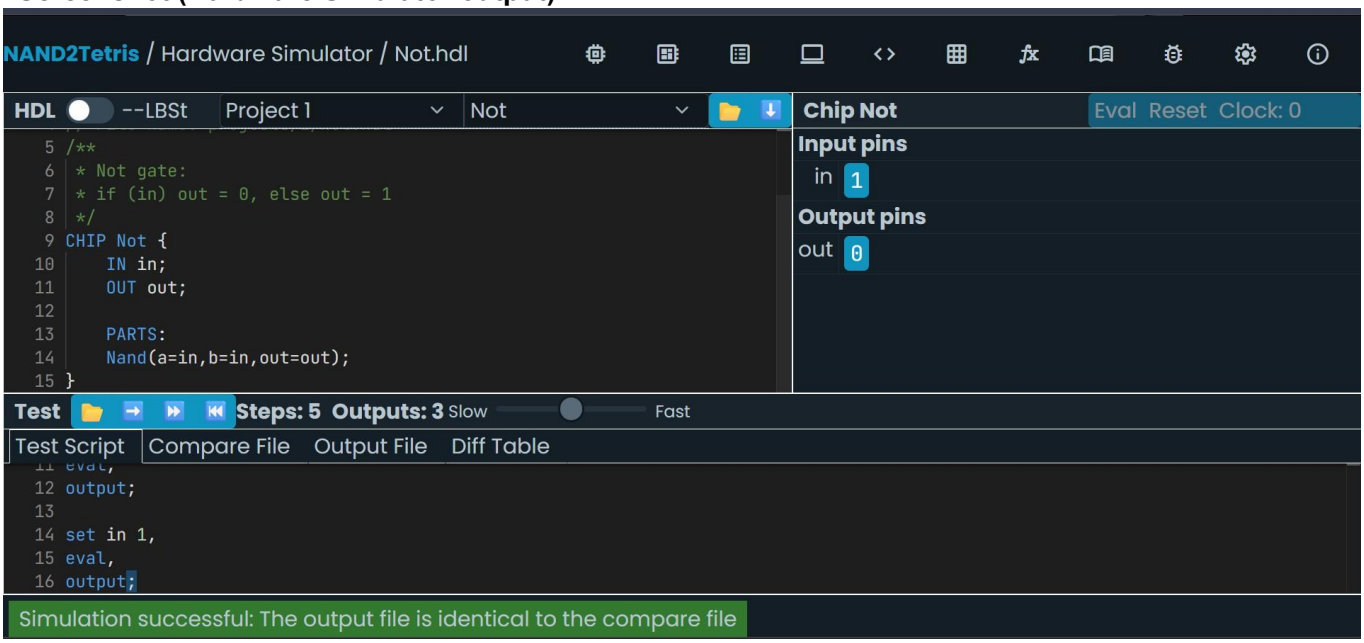

3. Or.hdl (Project 1)


Code:

```
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or.hdl
/**  * Or
gate:
```

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
* if (a or b) out = 1, else out = 0
 */
CHIP Or {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a, b=a,out=nand1);
    Nand(a=b, b=b, out=nand2);
    Nand(a=nand1 , b=nand2 , out=out );
}
```

Screenshot (Hardware Simulator output):

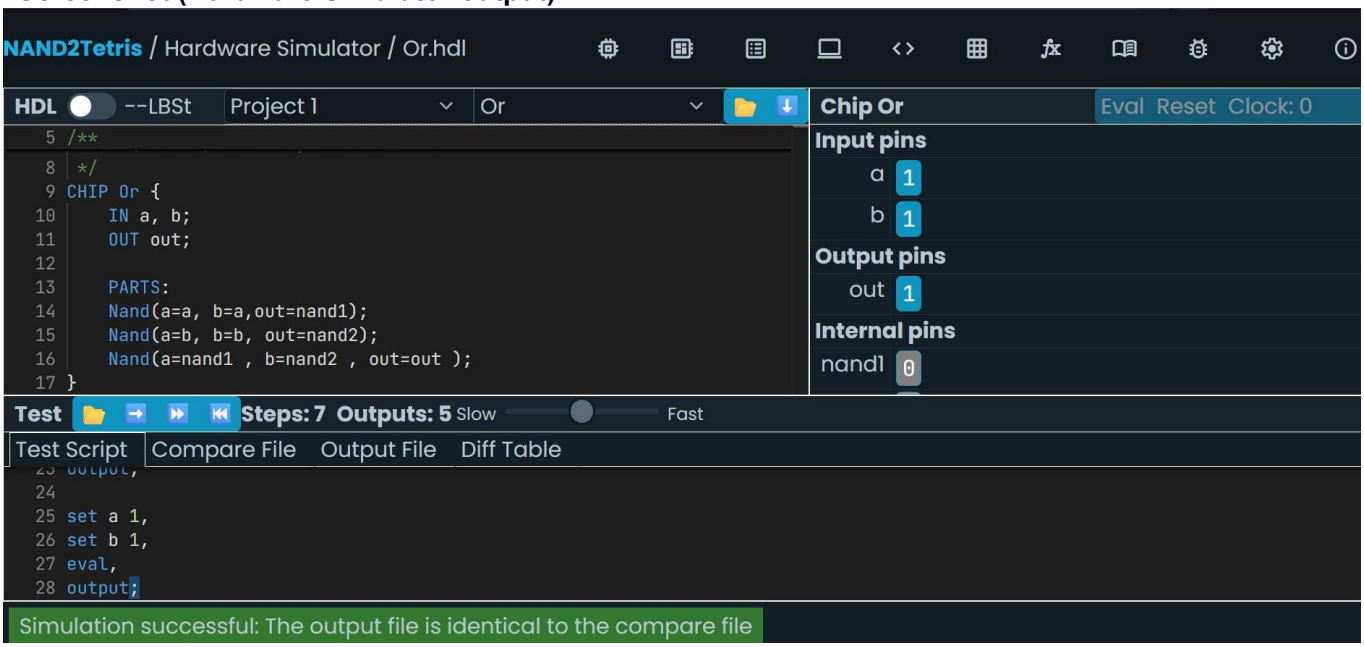

4. Xor.hdl (Project 1)


Code:

```
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Xor.hdl
/**  * Exclusive-or
gate:
* if ((a and Not(b)) or (Not(a) and b)) out = 1, else out = 0
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a , b=b , out=c );
```

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
    Nand(a=a , b=c , out=d );
    Nand(a=c , b=b , out=e );
    Nand(a=d , b=e , out=out );
}
```

Screenshot (Hardware Simulator output):

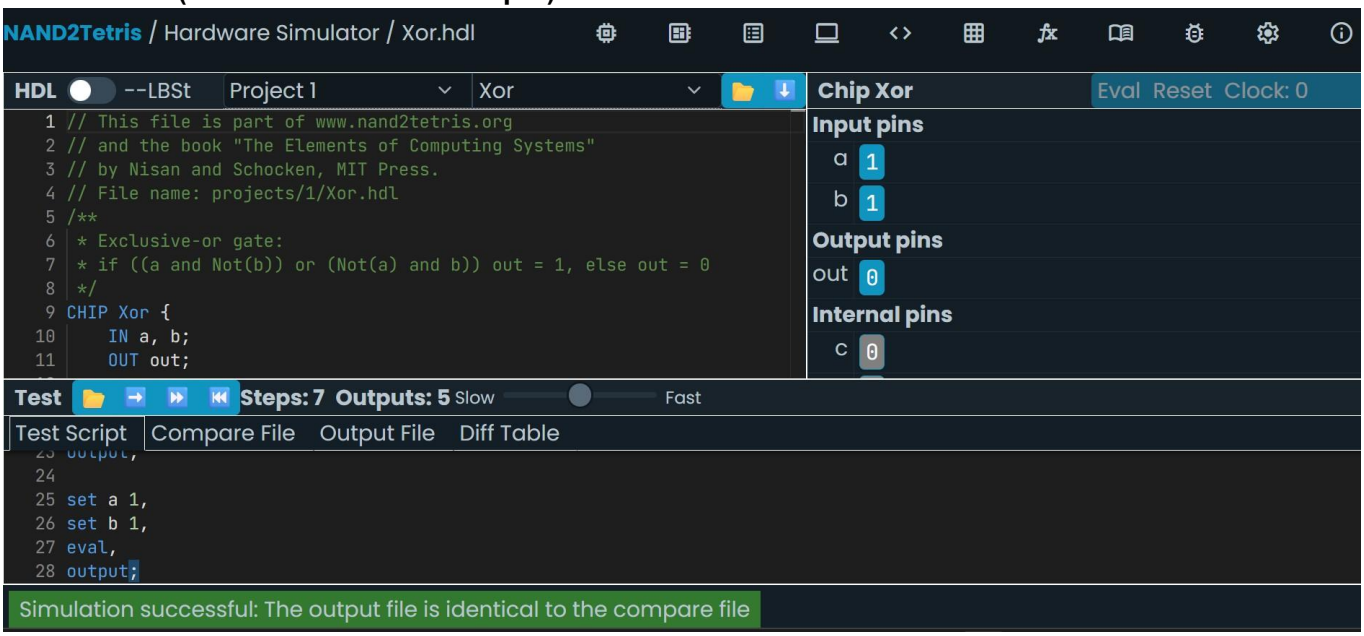

5. Mux.hdl (Project 1)

Code:


```
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux.hdl
/**  *
Multiplexor:
 * if (sel = 0) out = a, else out = b
 */
CHIP Mux {
    IN a, b, sel;
    OUT out;

    PARTS:
    Not(in=sel, out=asel);
    And(a=a, b=asel, out=a1);
    And(a=b, b=sel, out=b1);
    Or(a=a1, b=b1, out=out);

}
```

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
```

Screenshot (Hardware Simulator output):

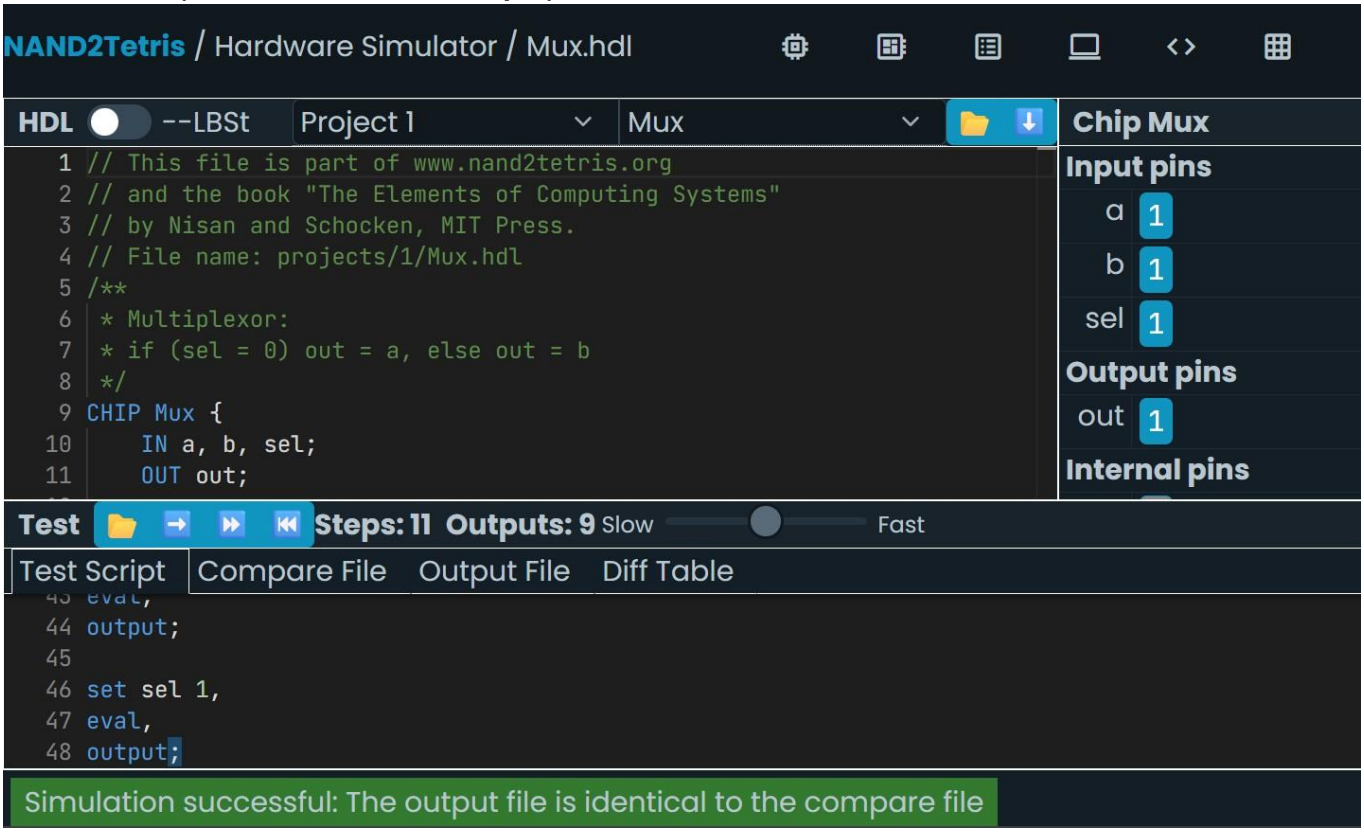


6. DMux.hdl (Project 1)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux.hdl
/**  *
Demultiplexor:
*          [a, b] = [in, 0] if sel = 0
*          [0, in] if sel = 1
 */
CHIP DMux {
    IN in, sel;
    OUT a, b;

    PARTS:
    Not(in=sel, out=nsel);
    And(a=in, b=nsel, out=a);
    And(a=in, b=sel, out=b);
}
```

Screenshot (Hardware Simulator output):

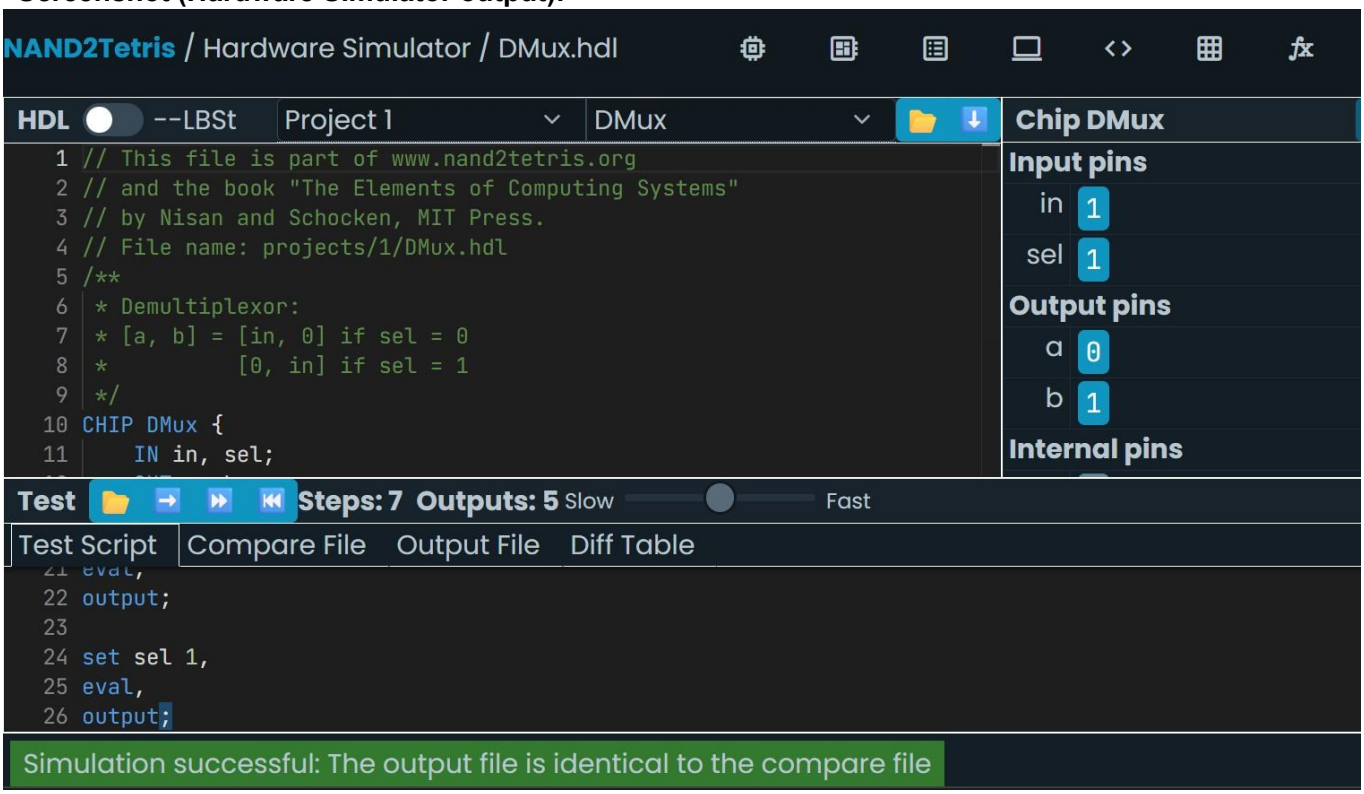

7. Not16.hdl (Project 1)


Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/01/Not16.hdl
```

```
/**  * 16-bit Not
gate:
*           for i = 0, ..., 15:
*           out[i] = Not(a[i])
 */
CHIP Not16 {
    IN in[16];
    OUT out[16];

    PARTS:
    Not(in=in[0] , out=out[0]);
    Not(in=in[1] , out=out[1]);
    Not(in=in[2] , out=out[2]);
    Not(in=in[3] , out=out[3]);
    Not(in=in[4] , out=out[4]);
    Not(in=in[5],  out=out[5]);
    Not(in=in[6],  out=out[6]);
    Not(in=in[7],  out=out[7]);
    Not(in=in[8],  out=out[8]);
    Not(in=in[9],  out=out[9]);
    Not(in=in[10], out=out[10]);
    Not(in=in[11], out=out[11]);
    Not(in=in[12], out=out[12]);
    Not(in=in[13], out=out[13]);
    Not(in=in[14], out=out[14]);
    Not(in=in[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

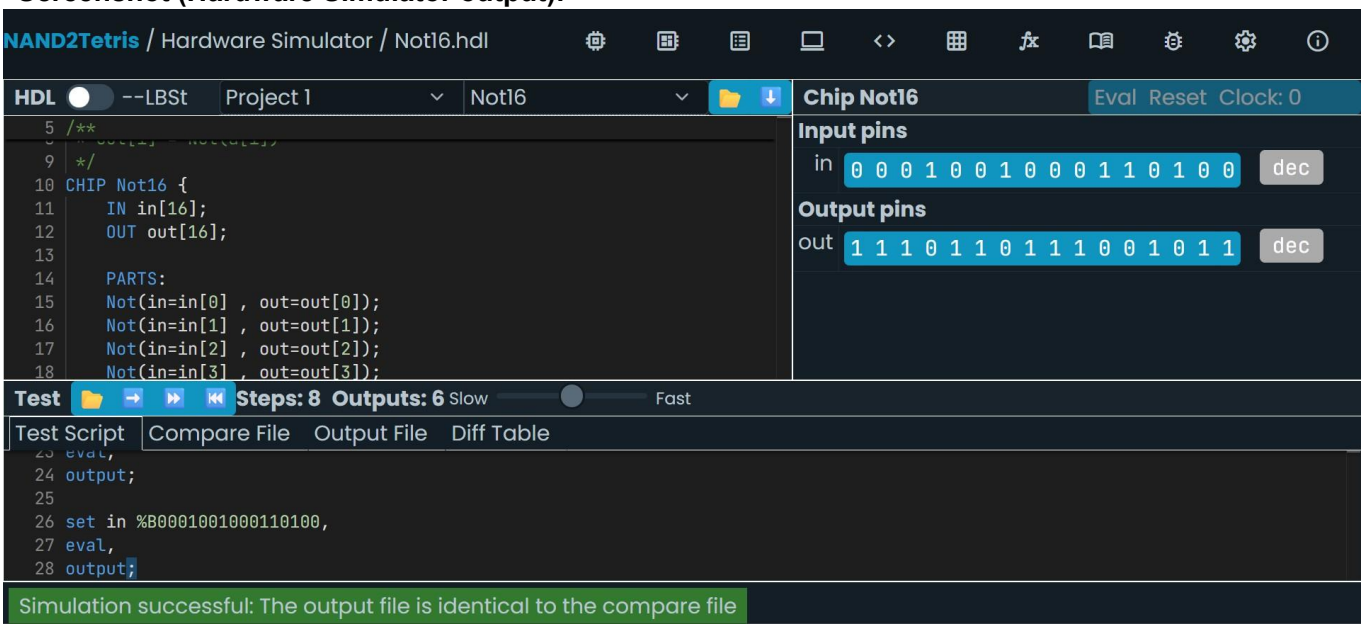

8. And16.hdl (Project 1)


Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/And16.hdl
```

```
/**  * 16-bit And
gate:
* for i = 0, ..., 15:
* out[i] = a[i] And b[i]
 */
CHIP And16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    And(a=a[0],  b=b[0],  out=out[0]);
    And(a=a[1],  b=b[1],  out=out[1]);
    And(a=a[2],  b=b[2],  out=out[2]);
    And(a=a[3],  b=b[3],  out=out[3]);
    And(a=a[4],  b=b[4],  out=out[4]);
    And(a=a[5],  b=b[5],  out=out[5]);
    And(a=a[6],  b=b[6],  out=out[6]);
    And(a=a[7],  b=b[7],  out=out[7]);
    And(a=a[8],  b=b[8],  out=out[8]);
    And(a=a[9],  b=b[9],  out=out[9]);
    And(a=a[10], b=b[10], out=out[10]);
    And(a=a[11], b=b[11], out=out[11]);
    And(a=a[12], b=b[12], out=out[12]);
    And(a=a[13], b=b[13], out=out[13]);
    And(a=a[14], b=b[14], out=out[14]);
    And(a=a[15], b=b[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

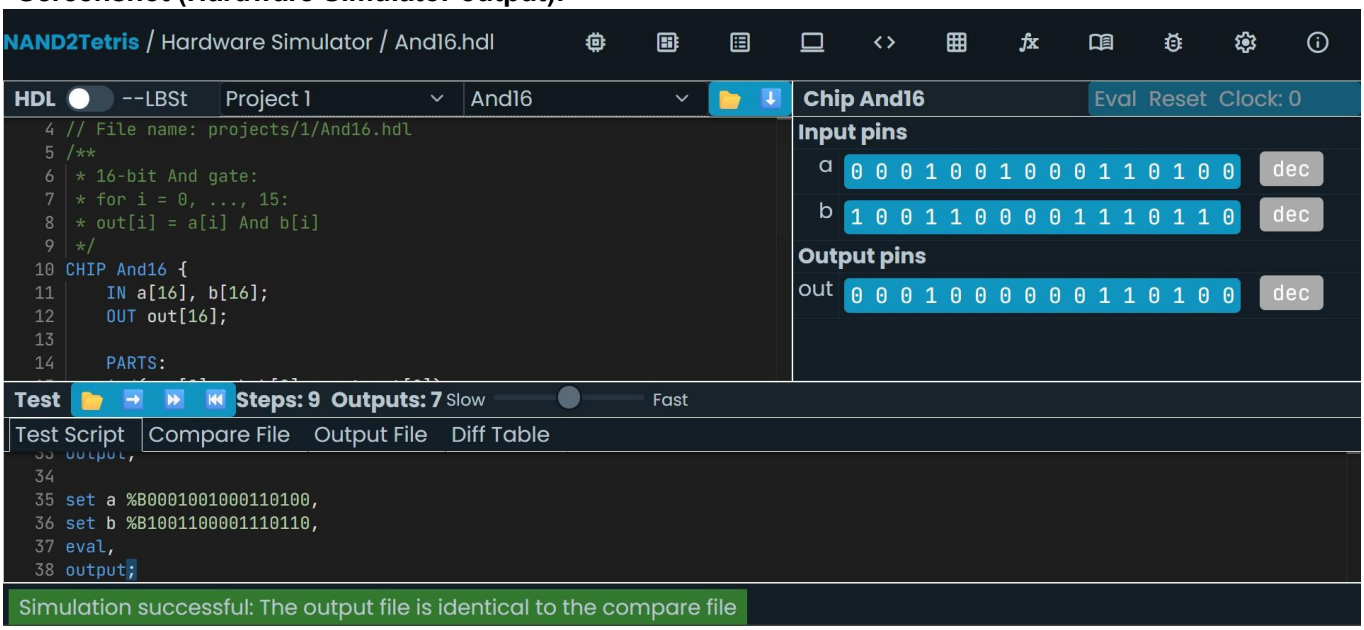


9. Or16.hdl (Project 1) Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or16.hdl
/**  * 16-bit Or
gate:
* for i = 0, ..., 15:
```

```
* out[i] = a[i] Or b[i]
 */
CHIP Or16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    Or(a=a[0],  b=b[0],  out=out[0]);
    Or(a=a[1],  b=b[1],  out=out[1]);
    Or(a=a[2],  b=b[2],  out=out[2]);
    Or(a=a[3],  b=b[3],  out=out[3]);
    Or(a=a[4],  b=b[4],  out=out[4]);
    Or(a=a[5],  b=b[5],  out=out[5]);
    Or(a=a[6],  b=b[6],  out=out[6]);
    Or(a=a[7],  b=b[7],  out=out[7]);
    Or(a=a[8],  b=b[8],  out=out[8]);
    Or(a=a[9],  b=b[9],  out=out[9]);
    Or(a=a[10], b=b[10], out=out[10]);
    Or(a=a[11], b=b[11], out=out[11]);
    Or(a=a[12], b=b[12], out=out[12]);
    Or(a=a[13], b=b[13], out=out[13]);
    Or(a=a[14], b=b[14], out=out[14]);
    Or(a=a[15], b=b[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

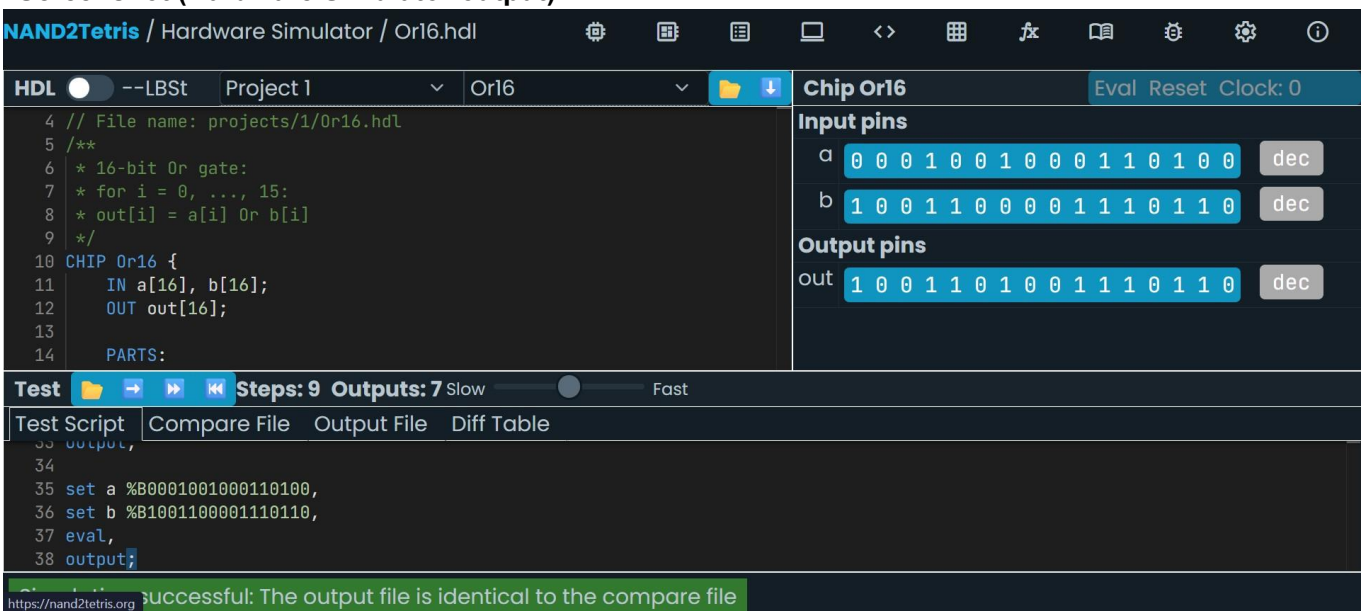

10. Mux16.hdl (Project 1)


Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux16.hdl
/**  * 16-bit
multiplexor:
* for i = 0, ..., 15:
* if (sel = 0) out[i] = a[i], else out[i] = b[i]
 */
```

```
CHIP Mux16 {
    IN a[16], b[16], sel;
    OUT out[16];

    PARTS:
    Mux(a=a[0],  b=b[0],  sel=sel, out=out[0]);
    Mux(a=a[1],  b=b[1],  sel=sel, out=out[1]);
    Mux(a=a[2],  b=b[2],  sel=sel, out=out[2]);
    Mux(a=a[3],  b=b[3],  sel=sel, out=out[3]);
    Mux(a=a[4],  b=b[4],  sel=sel, out=out[4]);
    Mux(a=a[5],  b=b[5],  sel=sel, out=out[5]);
    Mux(a=a[6],  b=b[6],  sel=sel, out=out[6]);
    Mux(a=a[7],  b=b[7],  sel=sel, out=out[7]);
    Mux(a=a[8],  b=b[8],  sel=sel, out=out[8]);
    Mux(a=a[9],  b=b[9],  sel=sel, out=out[9]);
    Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
    Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
    Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
    Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
    Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
    Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
}
```

Screenshot (Hardware Simulator output):

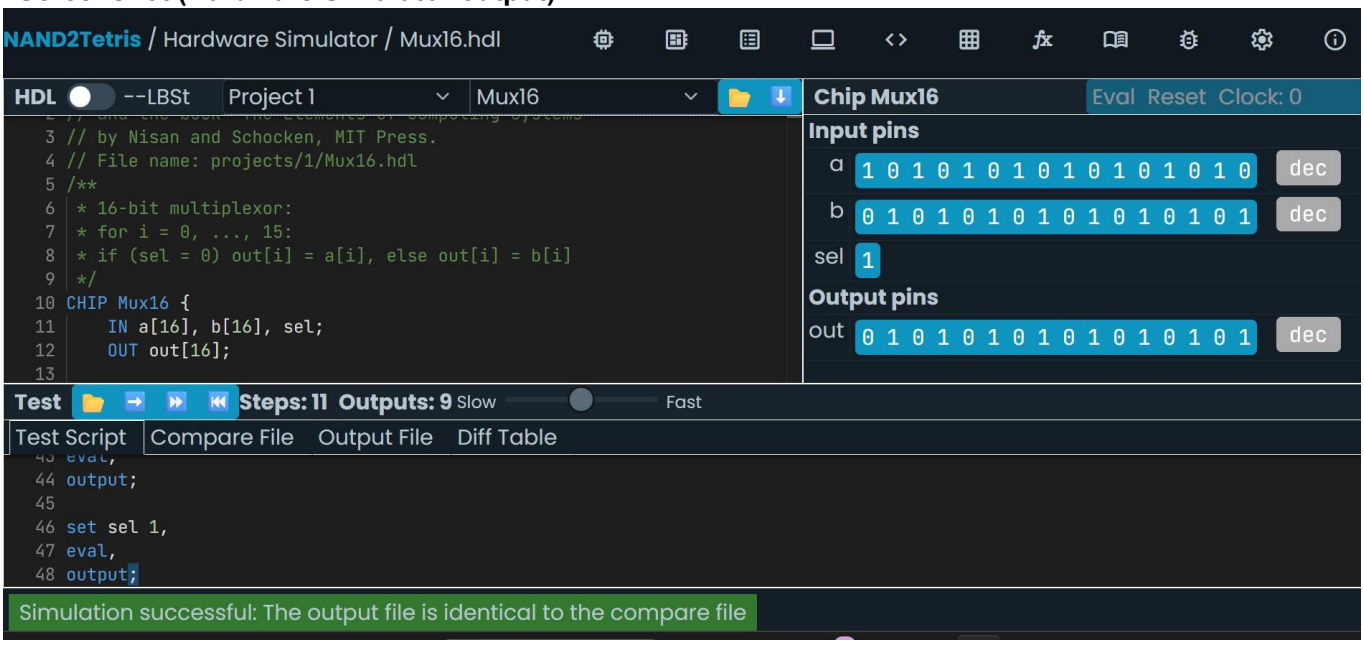

11. Or8Way.hdl (Project 1)


Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or8Way.hdl
/**  * 8-way Or
gate:
 * out = in[0] Or in[1] Or ... Or in[7]
 */
CHIP Or8Way {
    IN in[8];
```

```
    OUT out;

    PARTS:
    Or(a=in[0], b=in[1], out=w1);
    Or(a=w1, b=in[2], out=w2);
    Or(a=w2, b=in[3], out=w3);
    Or(a=w3, b=in[4], out=w4);
    Or(a=w4, b=in[5], out=w5);
    Or(a=w5, b=in[6], out=w6);
    Or(a=w6, b=in[7], out=out);
}
```

Screenshot (Hardware Simulator output):

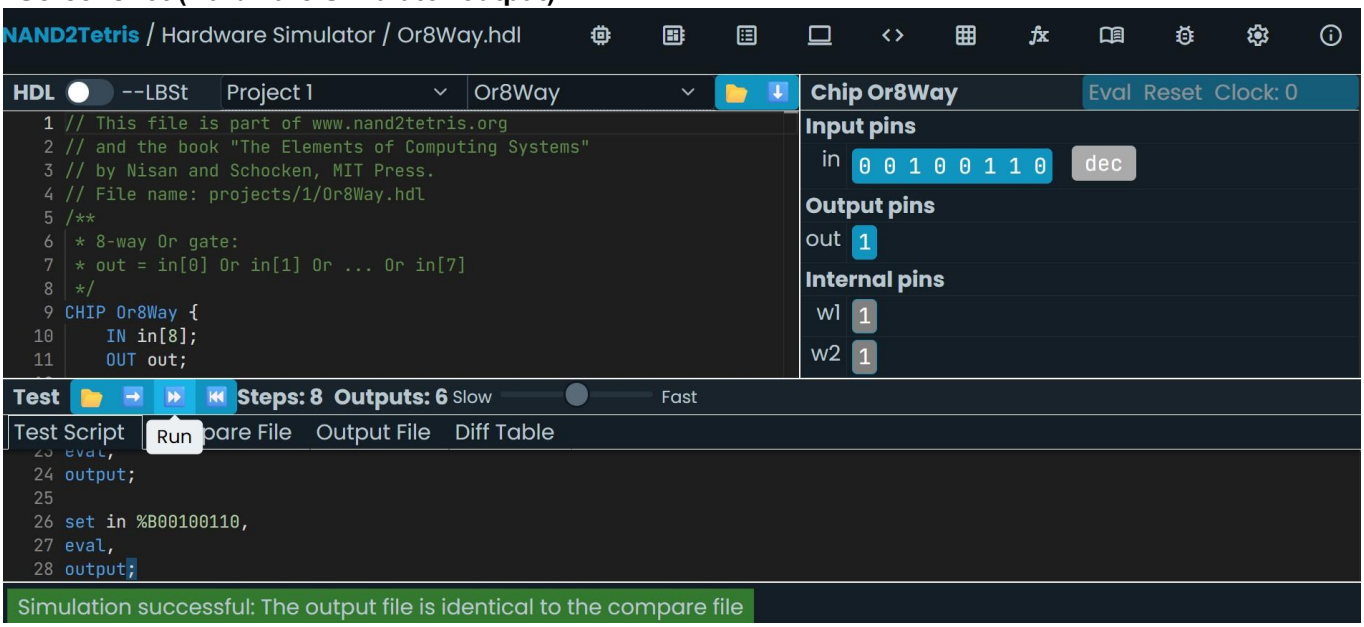


12. Mux4Way16.hdl (Project 1)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux4Way16.hdl
/**  * 4-way 16-bit
multiplexor:
*       out = a if sel = 00
*       b if sel = 01
*       c if sel = 10
*       d if sel = 11
 */
CHIP Mux4Way16 {
    IN a[16], b[16], c[16], d[16], sel[2];
    OUT out[16];

PARTS:
    Mux16(a=a, b=b, sel=sel[0], out=muxAB);
    Mux16(a=c, b=d, sel=sel[0], out=muxCD);
    Mux16(a=muxAB, b=muxCD, sel=sel[1], out=out);
}
```

Screenshot (Hardware Simulator output):

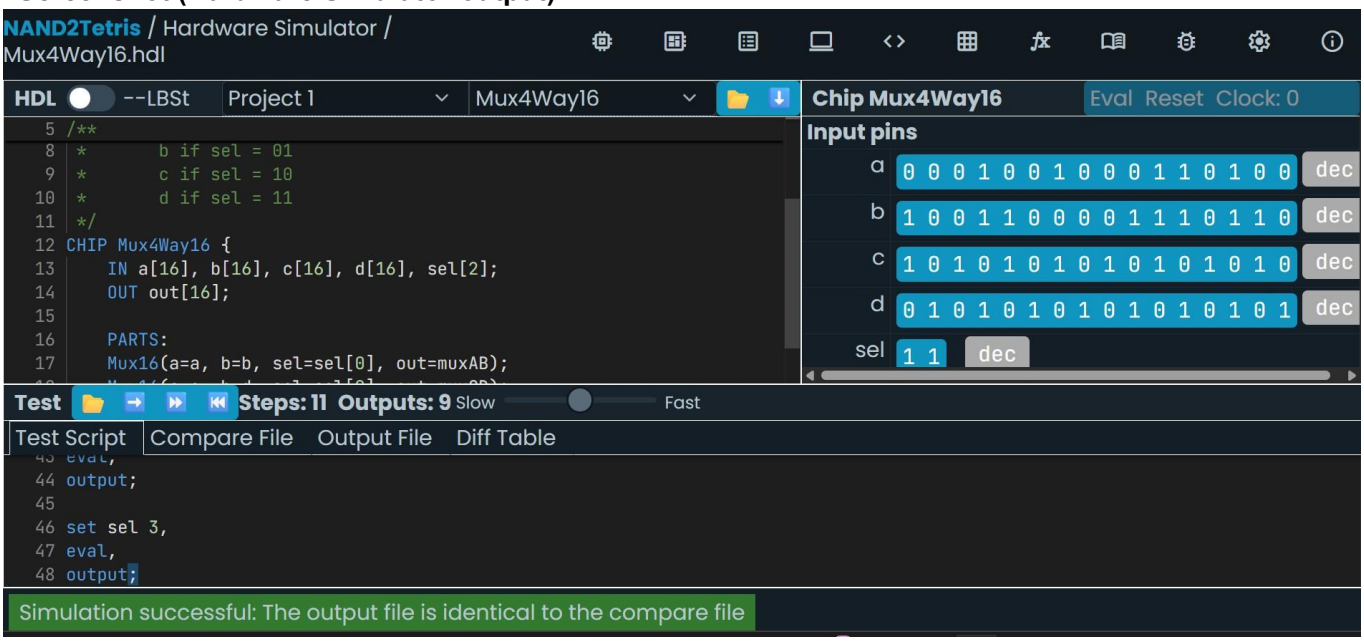


13. Mux8Way16.hdl (Project 1)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux8Way16.hdl
/**  * 8-way 16-bit
multiplexor:
*       out = a if sel = 000
*       b if sel = 001
*       c if sel = 010
*       d if sel = 011
*       e if sel = 100
*       f if sel = 101
*       g if sel = 110
*       h if sel = 111
 */
CHIP Mux8Way16 {     IN a[16],
b[16], c[16], d[16],        e[16],
f[16], g[16], h[16],
sel[3];     OUT out[16];

    PARTS:
    Mux4Way16(a=a, b=b, c=c, d=d, sel=sel[0..1], out=outABCD);
    Mux4Way16(a=e, b=f, c=g, d=h, sel=sel[0..1], out=outEFGH);
    Mux16(a=outABCD, b=outEFGH, sel=sel[2], out=out);
}
```

Screenshot (Hardware Simulator output):

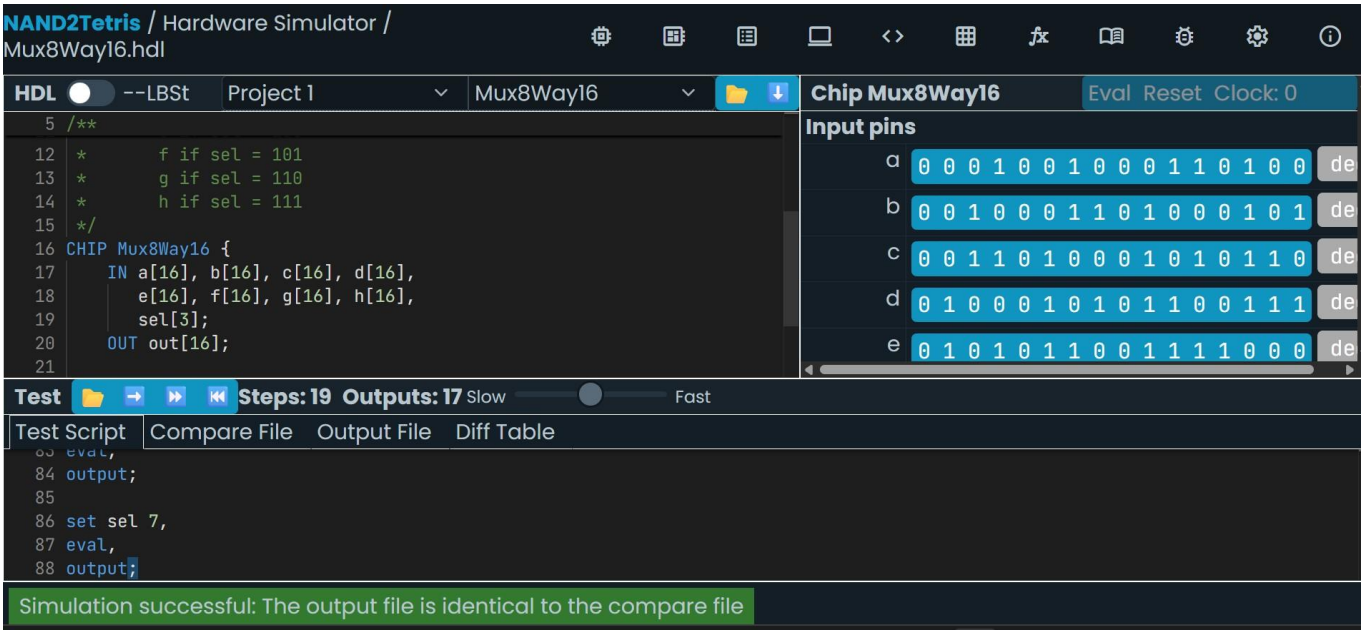


```
/**
*       f if sel = 101
*       g if sel = 110
*       h if sel = 111
*/
CHIP Mux8Way16 {
    IN a[16], b[16], c[16], d[16],
       e[16], f[16], g[16], h[16],
       sel[3];
    OUT out[16];

eval,
output;

set sel 7,
eval,
output;
```


14. DMux4Way.hdl (Project 1)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux4Way.hdl
/**  * 4-way
demultiplexor:
*                             [a, b, c, d] = [in, 0, 0, 0] if sel = 00
*                             [0, in, 0, 0] if sel = 01
*                             [0, 0, in, 0] if sel = 10
*                             [0, 0, 0, in] if sel = 11
 */
CHIP DMux4Way {
    IN in, sel[2];
    OUT a, b, c, d;

    PARTS:
    DMux(in=in, sel=sel[1], a=top, b=bottom);
    DMux(in=top,    sel=sel[0], a=a, b=b);
    DMux(in=bottom, sel=sel[0], a=c, b=d);
}
```

Screenshot (Hardware Simulator output):

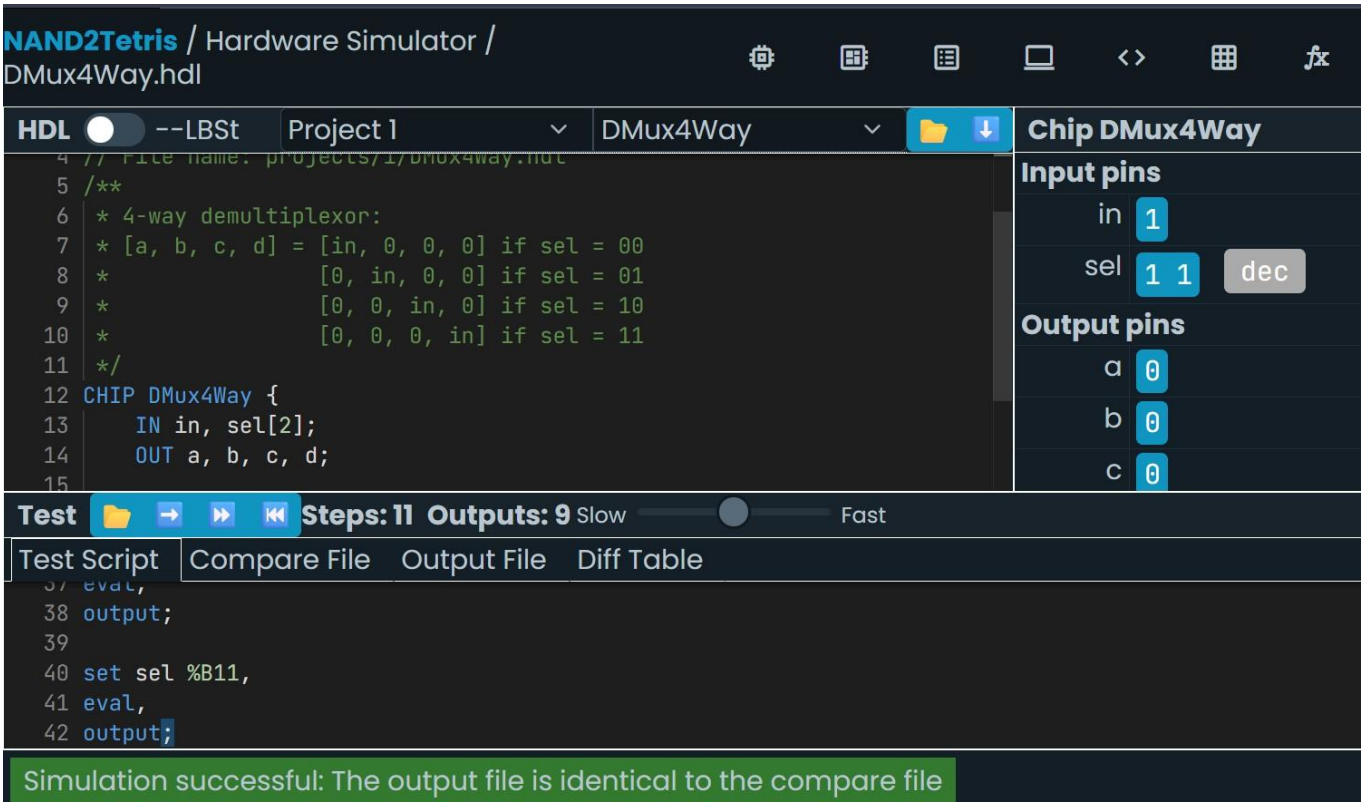


15. DMux8Way.hdl (Project 1)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux8Way.hdl
/**  * 8-way
demultiplexor:
*                           [a, b, c, d, e, f, g, h] = [in, 0,  0,  0,  0,  0,  0,  0] if sel =
                            000
*                           [0, in,  0,  0,  0,  0,  0,  0] if sel = 001
*                           [0,  0, in,  0,  0,  0,  0,  0] if sel = 010
*                           [0,  0,  0, in,  0,  0,  0,  0] if sel = 011
*                           [0,  0,  0,  0, in,  0,  0,  0] if sel = 100
*                           [0,  0,  0,  0,  0, in,  0,  0] if sel = 101
*                           [0,  0,  0,  0,  0,  0, in,  0] if sel = 110 *
                            [0,  0,  0,  0,  0,  0,  0, in] if sel = 111
 */
CHIP DMux8Way {
    IN in, sel[3];
    OUT a, b, c, d, e, f, g, h;

    PARTS:
    DMux(in=in, sel=sel[2], a=topGroup, b=bottomGroup);
    DMux4Way(in=topGroup,    sel=sel[0..1], a=a, b=b, c=c, d=d);
    DMux4Way(in=bottomGroup, sel=sel[0..1], a=e, b=f, c=g, d=h);
}
```

Screenshot (Hardware Simulator output):

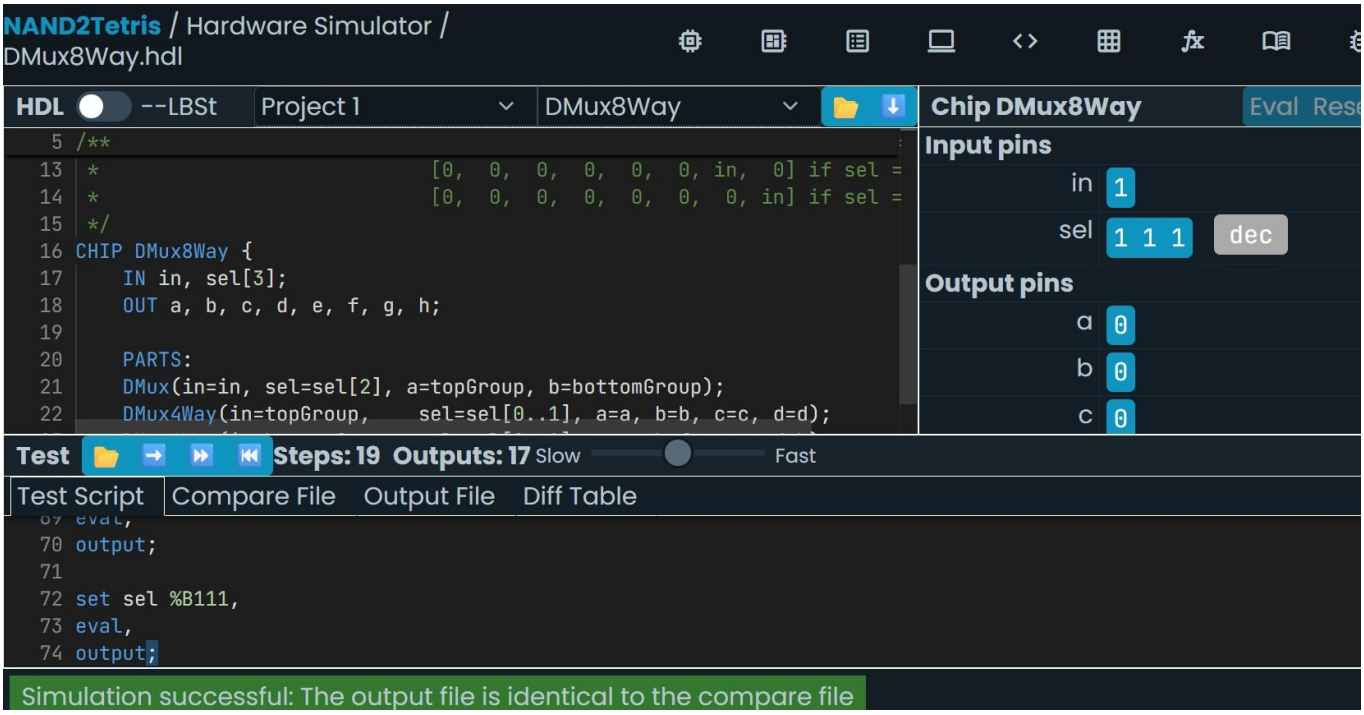


16. HalfAdder.hdl (Project 2)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/HalfAdder.hdl
/**  * Computes the sum of two
bits.
 */
CHIP HalfAdder {
    IN a, b;    // 1-bit inputs
OUT sum,    // Right bit of a + b
carry;  // Left bit of a + b

    PARTS:
    Xor(a=a, b=b, out=sum);
    And(a=a, b=b, out=carry);
}
```

Screenshot (Hardware Simulator output):

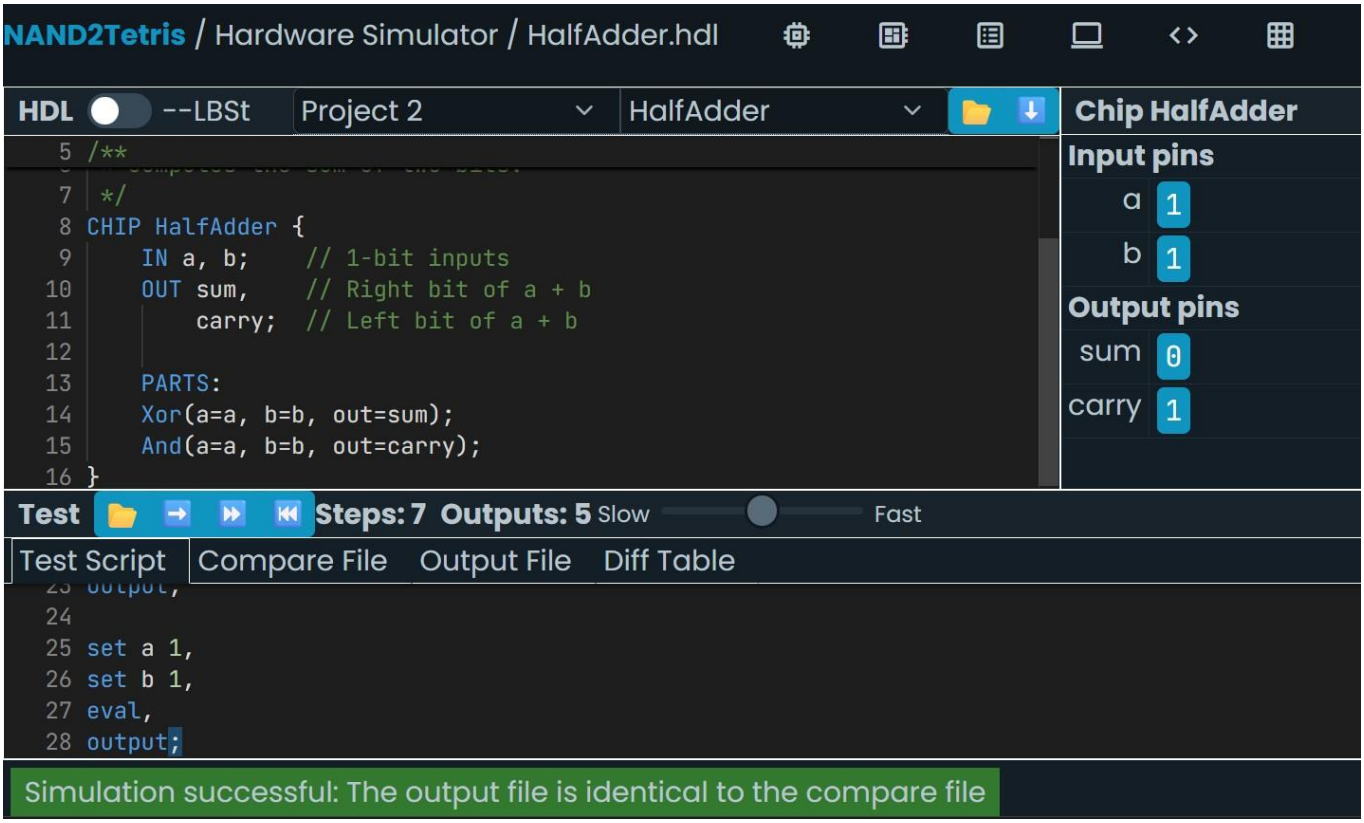


17. FullAdder.hdl (Project 2)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/FullAdder.hdl
/**  * Computes the sum of three
bits.
 */
CHIP FullAdder {
    IN a, b, c;  // 1-bit inputs     OUT
sum,     // Right bit of a + b + c
carry;   // Left bit of a + b + c

    PARTS:
    HalfAdder(a=a, b=b, sum=s1, carry=c1);
    HalfAdder(a=s1, b=c, sum=sum, carry=c2);
    Or(a=c1, b=c2, out=carry);
}
```

Screenshot (Hardware Simulator output):

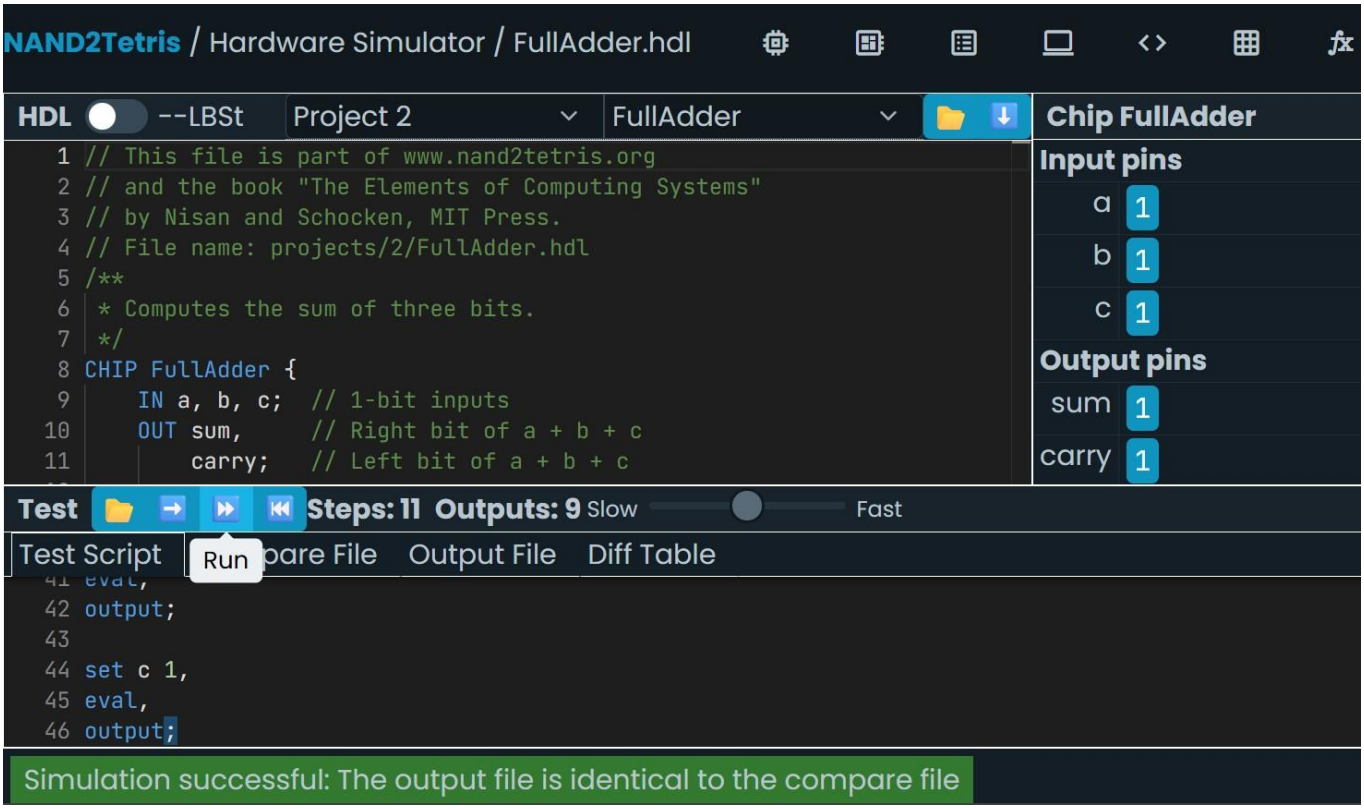

18. Add16.hdl (Project 2)


Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/Add16.hdl
/**  * 16-bit adder: Adds two 16-bit two's complement
values.
 * The most significant carry bit is ignored.
 */
CHIP Add16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    HalfAdder(a=a[0], b=b[0] , sum=out[0] , carry=c0 );
    FullAdder(a=a[1] , b=b[1] , c=c0 , sum=out[1] , carry=c1 );
    FullAdder(a=a[2] , b=b[2] , c=c1 , sum=out[2] , carry=c2);
    FullAdder(a=a[3] , b=b[3] , c=c2 , sum=out[3] , carry=c3 );
    FullAdder(a=a[4] , b=b[4] , c=c3 , sum=out[4] , carry=c4 );
    FullAdder(a=a[5] , b=b[5] , c=c4 , sum=out[5] , carry=c5 );
    FullAdder(a=a[6] , b=b[6] , c=c5 , sum=out[6] , carry=c6 );
    FullAdder(a=a[7] , b=b[7] , c=c6 , sum=out[7] , carry=c7 );
    FullAdder(a=a[8] , b=b[8] , c=c7 , sum=out[8] , carry=c8 );
    FullAdder(a=a[9] , b=b[9] , c=c8 , sum=out[9] , carry=c9);
    FullAdder(a=a[10] , b=b[10] , c=c9 , sum=out[10] , carry=c10 );
    FullAdder(a=a[11] , b=b[11] , c=c10 , sum=out[11] , carry=c11 );
    FullAdder(a=a[12] , b=b[12] , c=c11, sum=out[12] , carry=c12 );
    FullAdder(a=a[13] , b=b[13] , c=c12, sum=out[13] , carry=c13 );
    FullAdder(a=a[14] , b=b[14] , c=c13, sum=out[14] , carry=c14 );
    FullAdder(a=a[15] , b=b[15] , c=c14, sum=out[15] , carry=c15 );
```

```
}
```

Screenshot (Hardware Simulator output):

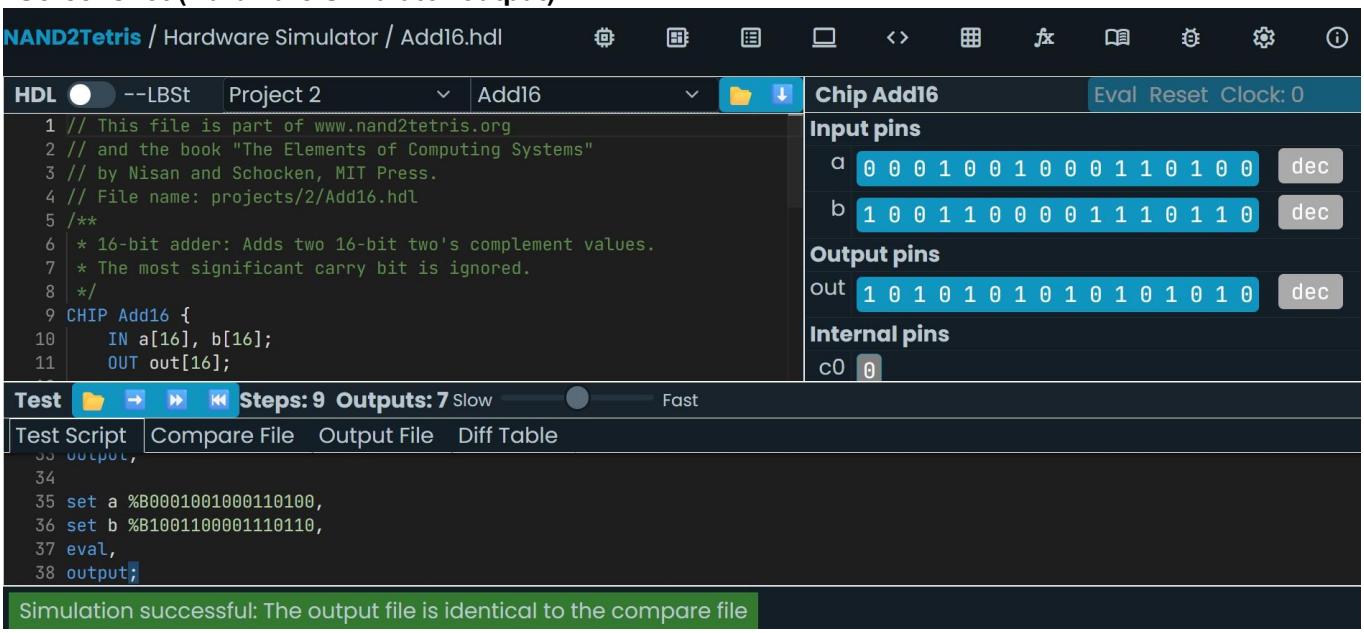


19. Inc16.hdl (Project 2)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/Inc16.hdl
/**  * 16-bit
incrementer:
 * out = in + 1
 */
CHIP Inc16 {
    IN in[16];
    OUT out[16];

    PARTS:
    Add16(a=in, b[0]=true, out=out);
}
```

Screenshot (Hardware Simulator output):

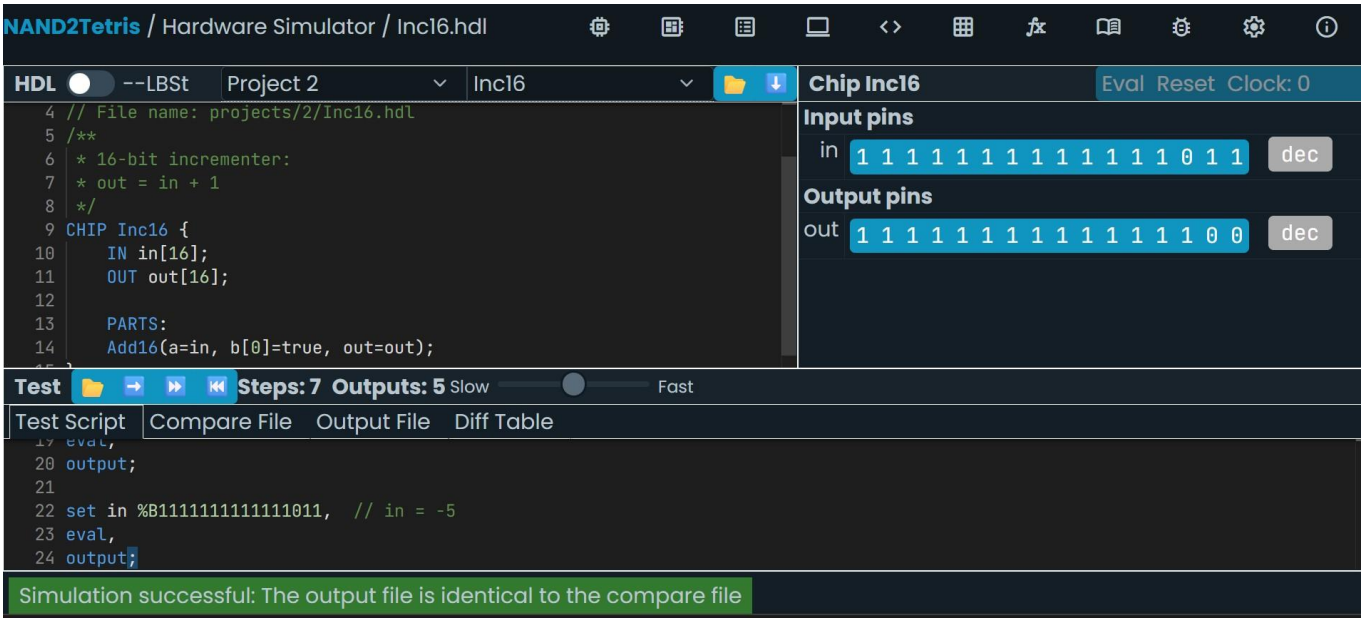

20. ALU.hdl (Project 2)

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/ALU.hdl
/**  * ALU (Arithmetic Logic
Unit):
*                Computes out = one of the following functions:
*                0, 1, -1,
*                x, y, !x, !y, -x, -y,
*                x + 1, y + 1, x - 1, y - 1,
*                x + y, x - y, y - x,
*                x & y, x | y
*                on the 16-bit inputs x, y, * according to the input bits zx, nx, zy, ny, f, no.
*                In addition, computes the two output bits:
*                if (out == 0) zr = 1, else zr = 0
*                if (out < 0)  ng = 1, else ng = 0
 */
// Implementation: Manipulates the x and y inputs
// and operates on the resulting values, as
follows:
// if (zx == 1) sets x = 0        // 16-bit constant
// if (nx == 1) sets x = !x       // bitwise not
// if (zy == 1) sets y = 0        // 16-bit constant
// if (ny == 1) sets y = !y       // bitwise not
// if (f == 1)  sets out = x + y  // integer 2's complement addition
// if (f == 0)  sets out = x & y  // bitwise and
// if (no == 1) sets out = !out   // bitwise not

CHIP ALU {     IN          x[16],
y[16],  // 16-bit inputs
zx, // zero the x input?         nx,
// negate the x input?         zy, //
zero the y input?         ny, //
negate the y input?
        f,  // compute (out = x + y) or (out = x &
y)?         no; // negate the out output?     OUT
out[16], // 16-bit output         zr,      // if (out
== 0) equals 1, else 0         ng;      // if (out <
0)  equals 1, else 0

    PARTS:
    // x zero / negate
      Mux16(a=x, sel=zx, out=x1);
```

```
        Not16(in=x1, out=negatedX);
    Mux16(a=x1, b=negatedX, sel=nx, out=x2);

        // y zero / negate
        Mux16(a=y, sel=zy, out=y1);
        Not16(in=y1, out=negatedY);
        Mux16(a=y1, b=negatedY, sel=ny, out=y2);


        // x + y OR x & y
        Add16(a=x2, b=y2, out=added);
        And16(a=x2, b=y2, out=xyAnd);
        Mux16(a=xyAnd, b=added, sel=f, out=result);

        // negate the output?
        Not16(in=result, out=negatedResult);
        Mux16(a=result, b=negatedResult, sel=no, out=out, out[15]=firstOut, out[0..7]=finalLeft,
    out[8..15]=finalRight);

        // output == 0 (zr)
        Or8Way(in=finalLeft, out=zrl);
        Or8Way(in=finalRight, out=zrr);
        Or(a=zrl, b=zrr, out=nzr);
        Not(in=nzr, out=zr);

        // output < 0 (ng)
    And(a=firstOut, b=true, out=ng);
    }
```

Screenshot (Hardware Simulator output):

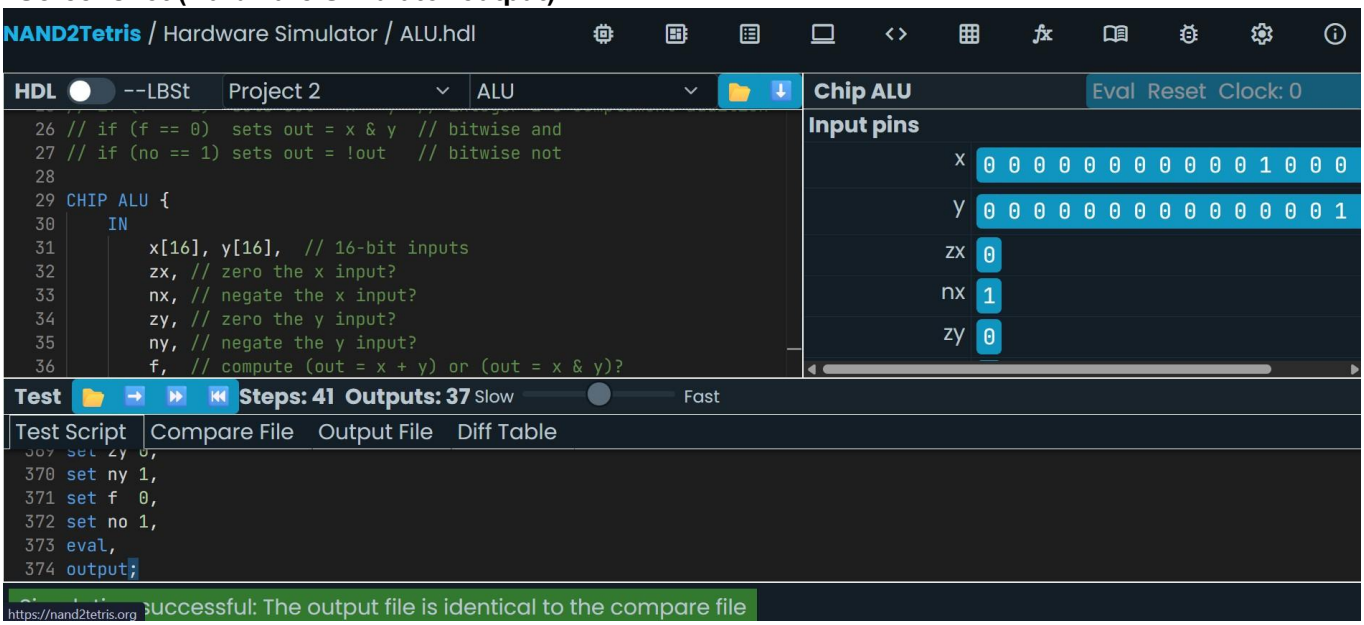

Thank You!